


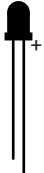
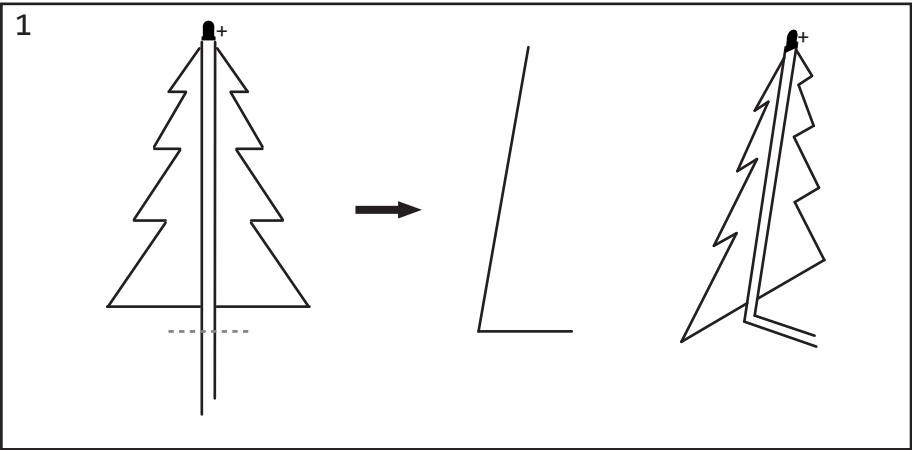
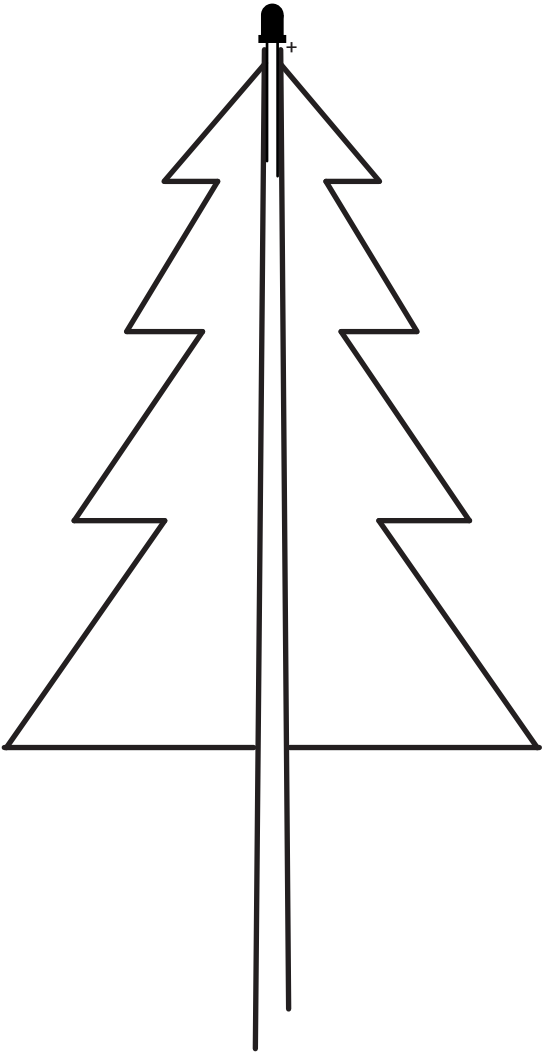
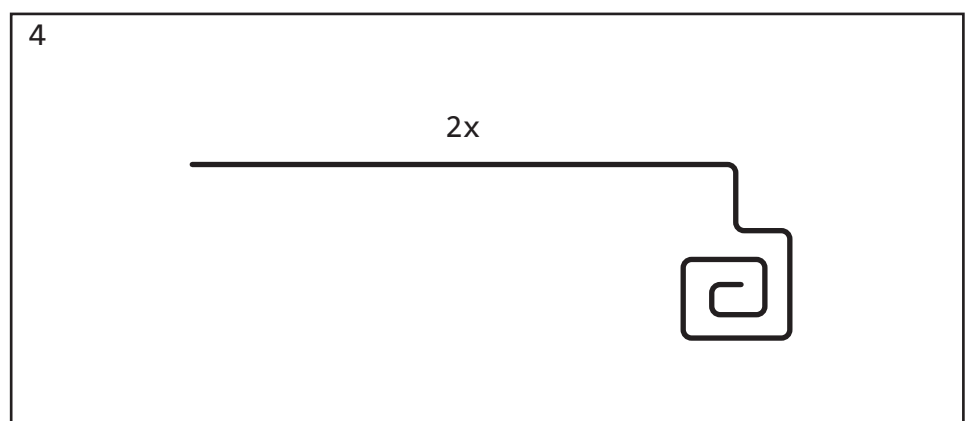
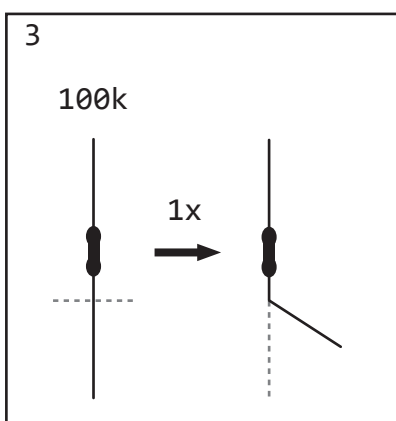
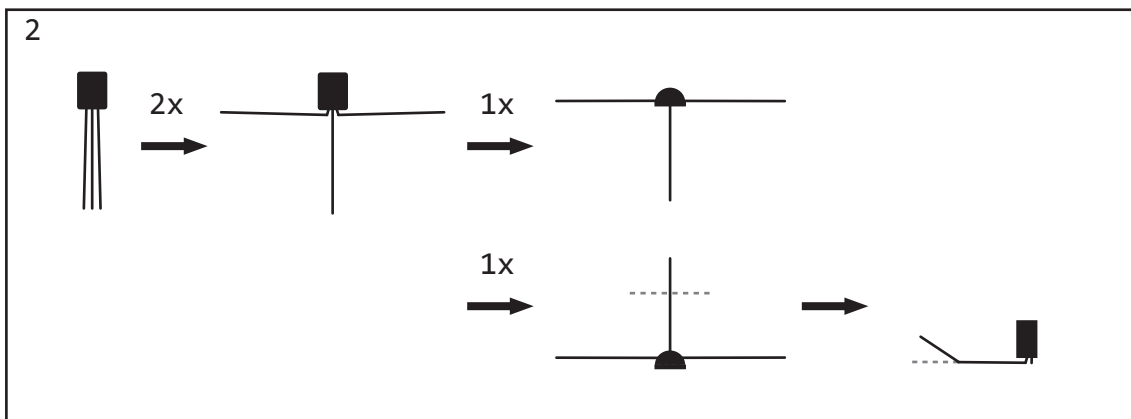
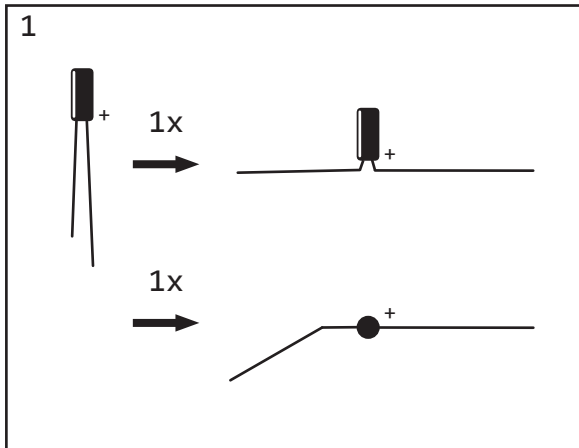
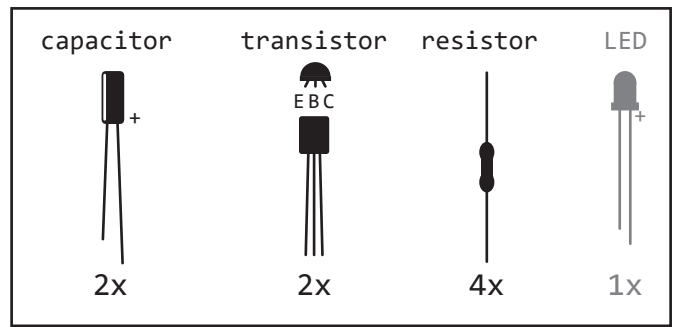


CHRISTMAS TREE


capacitor	transistor	resistor	LED
			
2x	2x	4x	1x







CHRISTMAS TREE




CHRISTMAS TREE

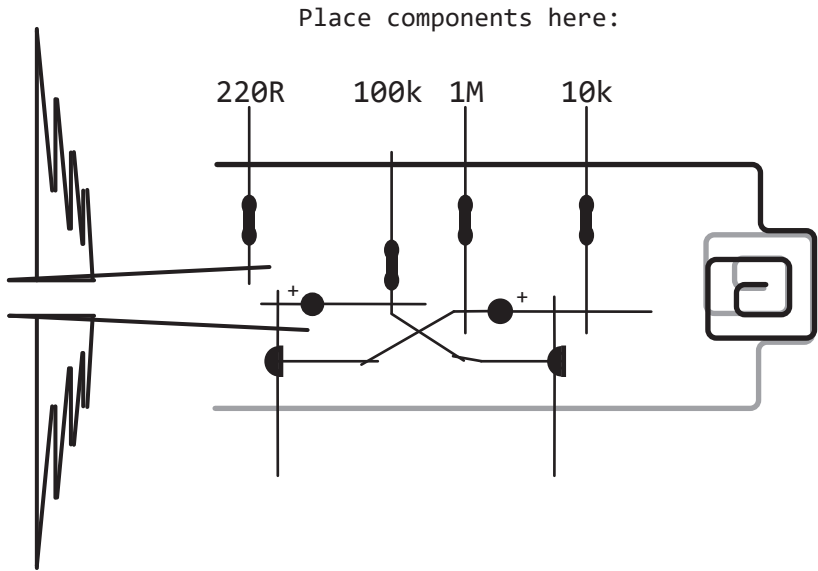

Follow these steps:

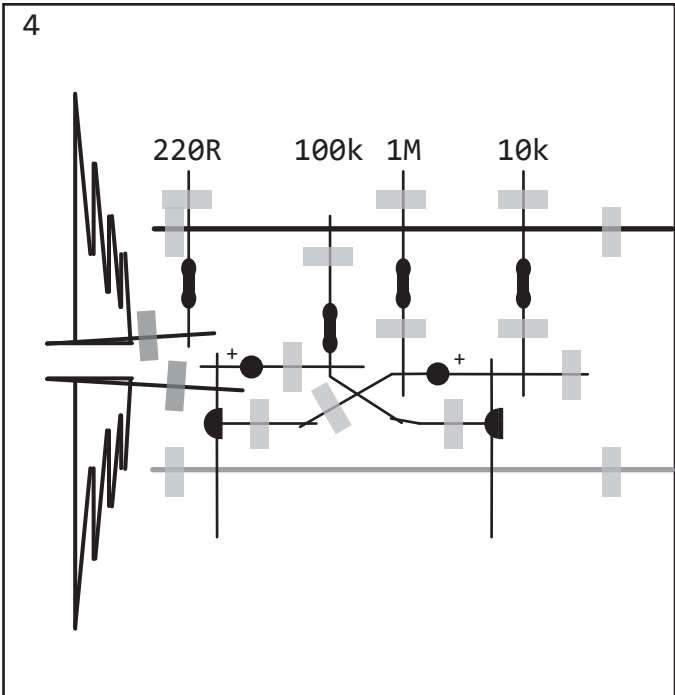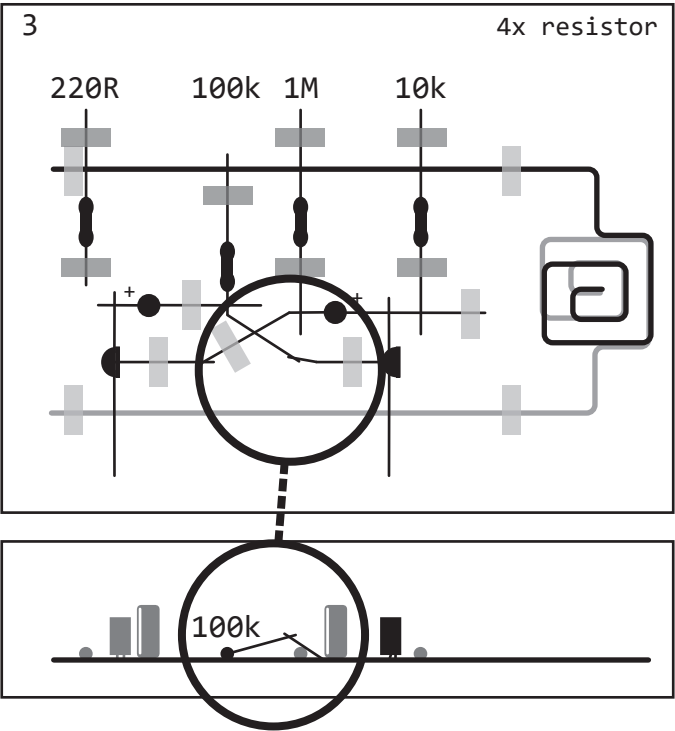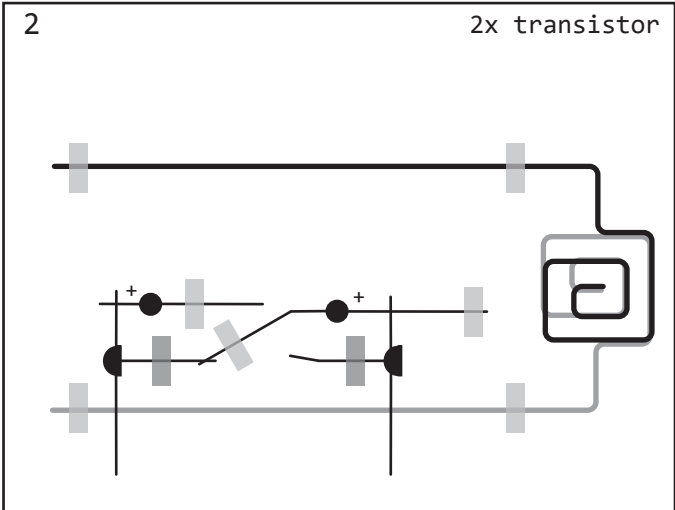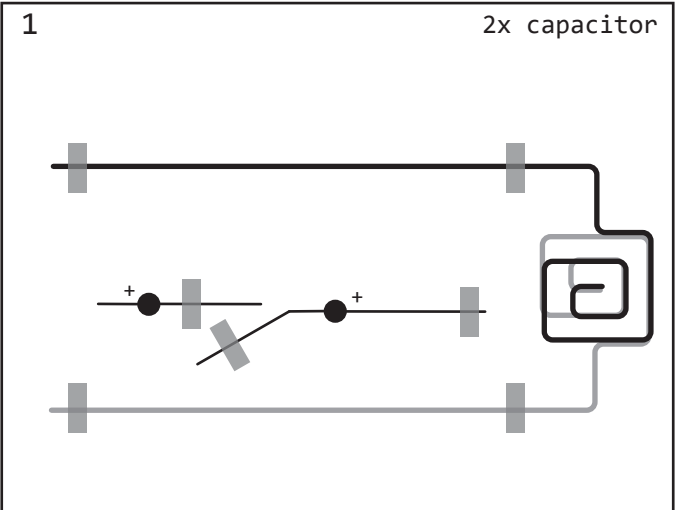

SCHEMATIC

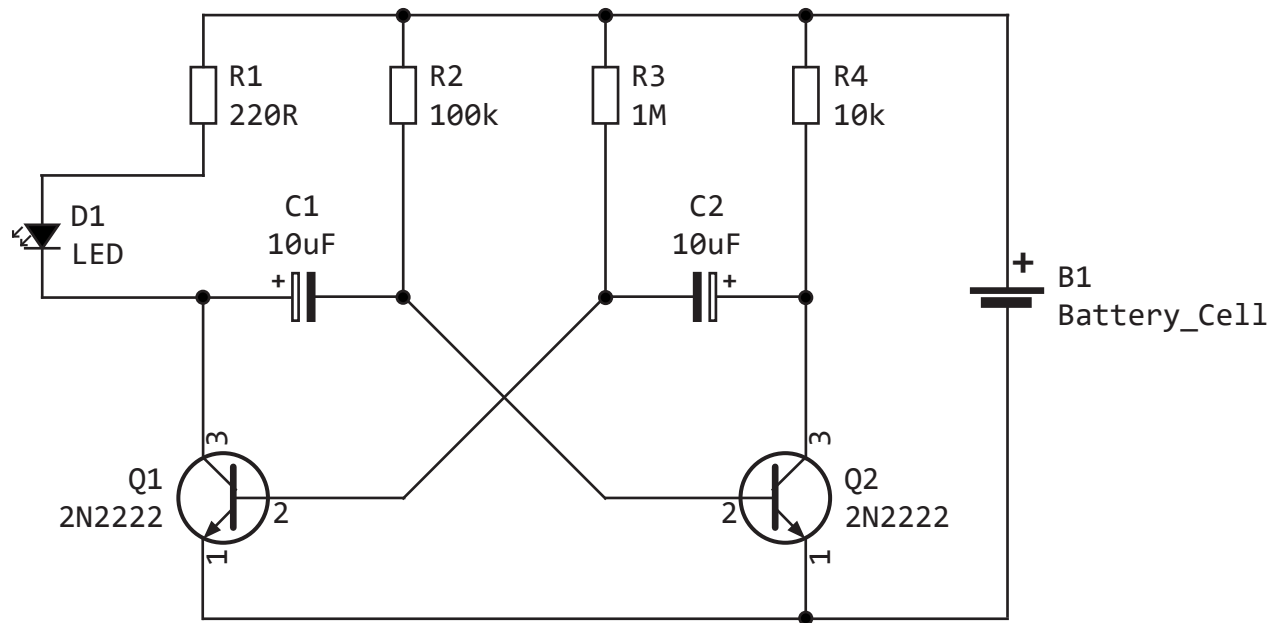

COMPONENTS

